

Values	Theory	Simulation
V <sub>R1</sub>	2,77V	2,78V
V <sub>R2</sub>	1,35V	1,33V
V <sub>R3</sub>	1,35V	1,33V
V <sub>R4</sub>	2,11V	2,14V
V <sub>R5</sub>	0,81V	0,81V
V <sub>R6</sub>	7,06V	7,08V
I <sub>R1</sub>	1,26mA	1,26mA
I <sub>R2</sub>	0,41mA	0,40mA
I <sub>R3</sub>	0,41mA	0,40mA
I <sub>R4</sub>	0,45mA	0,46mA
I <sub>R5</sub>	0,81mA	0,81mA
I <sub>R6</sub>	1,26mA	1,26mA
P <sub>R1</sub>	3,48W	3,502W
P <sub>R2</sub>	0,55W	0,53W
P <sub>R3</sub>	0,55W	0,53W
P <sub>R4</sub>	0,95W	0,98W
P <sub>R5</sub>	0,66W	0,66W
P <sub>R6</sub>	8,89W	8,92W

$$P = IV$$

$$P_1 = (1,26\text{mA})(2,78\text{V})$$

$$= 3,502\text{W}$$

$$P_2 = (0,40\text{mA})(1,33\text{V})$$

$$= 0,53\text{W}$$

$$P_4 = (0,46\text{mA})(2,14\text{V})$$


$$= 0,98\text{W}$$

$$P_5 = (0,81\text{mA})(0,81\text{V})$$

$$= 0,66\text{W}$$

$$P_6 = (1,26\text{mA})(7,08\text{V})$$

$$= 8,92\text{W}$$

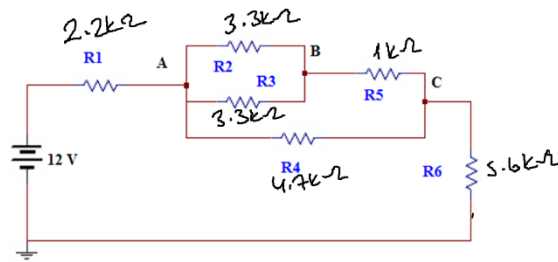

$R_1 = 2.2 \text{ k}\Omega$ ,  
 $R_4 = 4.7 \text{ k}\Omega$ ,

$R_2 = 3.3 \text{ k}\Omega$ ,  
 $R_5 = 1.0 \text{ k}\Omega$

$R_3 = 3.3 \text{ k}\Omega$ ,  
 $R_6 = 5.6 \text{ k}\Omega$

$$P = I^2 \cdot R$$

$$P_1 = (1.26 \text{ mA})^2 (2.2 \text{ k}\Omega) = 3.49 \text{ W}$$

$$P_2 = P_3 = (0.41 \text{ mA})^2 (3.3 \text{ k}\Omega) = 0.55 \text{ W}$$

$$P_4 = (0.45 \text{ mA})^2 (4.7 \text{ k}\Omega) = 0.95 \text{ W}$$

$$P_5 = (0.81 \text{ mA})^2 (1 \text{ k}\Omega) = 0.66 \text{ W}$$

$$P_6 = (1.26 \text{ mA})^2 (5.6 \text{ k}\Omega) = 8.89 \text{ W}$$

$$R_2 \parallel R_3 = \frac{3.3 \text{ k}\Omega}{2} = 1.65 \text{ k}\Omega$$

$$R_5 \parallel R_{eq} = (1.65 + 1) \text{ k}\Omega = 2.65 \text{ k}\Omega$$

$$R_4 \parallel \frac{(2.65 \times 4.7) \text{ k}\Omega}{(2.65 + 4.7)} = 1.63 \text{ k}\Omega$$

$$R_1 \parallel R_6 = \frac{2.2 \text{ k}\Omega}{1.63 + 2.2 + 5.6 \text{ k}\Omega} = 9.48 \text{ k}\Omega \rightarrow R_{eq}$$

$$U = i \cdot R$$

$$12 \text{ V} = i \cdot 9.48 \text{ k}\Omega$$

$$i_{eq} = 1.26 \text{ mA}$$

$$\textcircled{2} \quad \frac{2.65 \text{ k}\Omega}{4.7 \text{ k}\Omega} = 0.56 \text{ k}\Omega \rightarrow \text{ratio}$$

$$1.56 \text{ k}\Omega \times 1.26 \text{ mA} \quad ? = 0.81 \text{ mA} \quad \uparrow i_2 = i_3 + i_4$$

$$1.56 \text{ k}\Omega \quad 1.26 \text{ mA} \quad ? = 0.45 \text{ mA} \quad \uparrow i_4$$

$$i_2 + i_3 = 0.81$$

$$i_2 = i_3 = 0.41 \text{ mA}$$

$$i_6 = 0.81 + 0.45 \quad i_5 = 0.81 \text{ mA}$$

$$= 1.26 \text{ mA}$$

$$U = i \cdot R$$

$$U_1 = (1.26 \text{ mA}) (2.2 \text{ k}\Omega) = 2.77 \text{ V}$$

$$U_3 = U_2 = (0.41 \text{ mA}) (3.3 \text{ k}\Omega) = 1.35 \text{ V}$$

$$U_4 = (0.45 \text{ mA}) (4.7 \text{ k}\Omega) = 2.11 \text{ V}$$

$$U_5 = (0.81 \text{ mA}) (1 \text{ k}\Omega) = 0.81 \text{ V}$$

$$U_6 = (1.26 \text{ mA}) (5.6 \text{ k}\Omega) = 7.06 \text{ V}$$

### **PART III : Conclusion**

Because of the resistor's tolerance we see deviations. Tolerance cause different values and because of this values our calculations and simulation results are different.

